

**B.Sc. Part—II Semester—III Examination**  
**ELECTRONICS**  
**(Electronics Devices and Circuits)**

Time : Three Hours]

[Maximum Marks : 80

**Note** :—(1) Question No. 1 is compulsory.  
(2) Draw neat diagram wherever necessary.

1. (A) Fill in the blanks with correct word :— 2
- (i) The oscillator uses \_\_\_\_\_ feedback.
  - (ii) Input impedance of ideal OPAMP is \_\_\_\_\_.
  - (iii) In ideal Op-AMP value of output impedance is \_\_\_\_\_.
  - (iv) The conduction angle of Class B amplifier is \_\_\_\_\_ degree.
- (B) Choose correct alternative :— 2
- (i) Op-AMP IC741 has total \_\_\_\_\_ pins.  
(a) 2 (b) 6  
(c) 14 (d) 8
  - (ii) The  $h_{fe}$  is given by :  
(a)  $\partial I_C / \partial I_B$  (b)  $\partial I_B / \partial I_C$   
(c)  $\partial V_{CE} / \partial I_C$  (d)  $\partial V_{BE} / \partial V_{CE}$
  - (iii) The regenerative comparator is also known as \_\_\_\_\_.  
(a) Schmitt trigger (b) Monostable  
(c) Astable (d) None
  - (iv) Multistage amplifier are used in order to achieve \_\_\_\_\_.  
(a) Low Gain (b) High Gain  
(c) Frequency response (d) All of the above
- (C) Answer the following question each in one sentence only :—
- (i) What is feedback ?
  - (ii) Define Bandwidth in case of RC coupled amplifier.
  - (iii) Define power amplifier.
  - (iv) What is A/D converter ? 4

**EITHER**

2. (A) What is tuned amplifier ? Give its advantages. 3  
(B) Draw circuit diagram of single tuned amplifier. 3  
(C) Explain construction and operation of two stage R-C coupled amplifier with circuit diagram. 6

**OR**

- (P) Explain the determination of h-parameter. 4  
(Q) Draw hybrid equivalent circuit for transistor amplifier. Derive the expression for :  
(i) Input impedance  
(ii) Output impedance for a single stage CE transistor amplifier. 8

- EITHER**
3. (A) Give the classification of power amplifier. Explain. 4  
(B) Explain construction and operation of Class B push pull amplifier. Derive the expression for its efficiency. 8
- OR**
- (P) State the difference between Class A and Class B power amplifier. 4  
(Q) Explain construction and working of transformer coupled Class A amplifier. Show the efficiency of transformer coupled resistive load Class A power amplifier is 50%. 8
- EITHER**
4. (A) State the difference between amplifier and oscillator. 3  
(B) Deduce an equation for voltage gain of an amplifier using negative feedback. 6  
(C) Amplifier's total harmonic distortion is reduced from 8% to 2% when 5% negative feedback is used. Calculate the voltage gain of the amplifier with and without feedback. 3
- OR**
- (P) Explain the construction and working of Hartley oscillator. 6  
(Q) Draw a circuit diagram of RC-Phase shift oscillator and explain its working. 6
- EITHER**
5. (A) Draw the block diagram of IC Op-Amp and explain the function of each block. 6  
(B) Explain the working of Op-Amp as inverting amplifier. Derive the expression for gain. 6
- OR**
- (P) Explain the terms :—  
(i) CMRR  
(ii) Slew rate  
(iii) Open loop gain 6  
(Q) Explain the working of Op-Amp as integrator. 6
- EITHER**
6. (A) Explain the operation of Op-Amp as an astable multivibrator. 6  
(B) Draw a possible computer set up required for solving following simultaneous equation  $3x + y = 6$  and  $2x + 5y = 7$ . Write the necessary steps. 6
- OR**
- (P) Draw the circuit of monostable multivibrator using Op-Amp. Explain its operation. 6  
(Q) Explain how Op-Amp is used as harmonic oscillator. Write necessary steps. 6
- EITHER**
7. (A) Give the difference between A/D and D/A converter. 4  
(B) Explain the principle and working of successive approximation type A/D converter with suitable diagram. 8
- OR**
- (P) Explain the needs of ADC and DAC. 3  
(Q) Explain the terms : —  
(i) Accuracy  
(ii) Resolution in D/A converter. 3  
(R) Explain the construction and working of weighted resistor D/A converter. 6